

Memory Design

In digital system design, the usage of memory elements is unavoidable. In some of the systems, data can be pre-stored in a constant memory. Memory elements can be used as temporary storage of intermediate data. Memory elements can also be used to realize any logic function.

In this tutorial, realization of different types of memory blocks using Verilog is discussed. Though there are only 2 types of memory block exists, we divided memory blocks into four types according to their usage. Those are

1. Controlled Register
2. Single port Read Only Memory (ROM)
3. Single port Random Access Memory (RAM)
4. Dual port memory elements

Controlled Register

Controlled registers can be considered as basic elements of larger memory blocks. It has a Control Enable (CE) input along with reset, preset inputs. When CE is high, data is loaded or data is written into this control register and output is remain unchanged until any change in CE input. The usage of control registers is useful when we want to store a data vector or a scalar data. This saves the limited numbers of inbuilt memory blocks. The block diagram of a control register is shown below.

 


Fig. 1: Controlled Register

Single port Read Only Memory (ROM)

Read Only Memory (ROM) is a constant memory. The usage of this type of memory is obvious. ROM can be used to hold initial data for a system to start. A simple Verilog code for a single port ROM is shown below. Here initial data are loaded in the array locations using the case statement. The *en* input is sometimes optional but it is preferred to use *en* input to disable the memory block when not in use.



Fig. 2: Single Port ROM

```

module rom(clk,adres,data_out,en);

input clk,en;

input [2:0] adres;

output reg [7:0] data_out;

reg [7:0] mem [0:7];

initial begin data_out = 8'b00000000; end

always @ (adres)

case (adres)

3'b000 : mem[adres] = 8'b00000001;

3'b001 : mem[adres] = 8'b00000010;

3'b010 : mem[adres] = 8'b00000011;

3'b011 : mem[adres] = 8'b00000100;

3'b100 : mem[adres] = 8'b00000101;

3'b101 : mem[adres] = 8'b00000110;

3'b110 : mem[adres] = 8'b00000111;

3'b111 : mem[adres] = 8'b00001000;

default : mem[adres] = 8'b00000000;

endcase

always@(posedge clk)

begin

if(en)begin

data_out <= mem[adres];

end else

data_out <= data_out;

end

endmodule

```

Single port Random Access Memory (RAM)

Random Access Memory (RAM) blocks are used to store data temporarily in digital system. In a single port RAM, writing and reading can be done through one port only. It has one *en* input and *we* input. When *en* and *we* are both high, data are written into RAM and if *en* is high but *we* is low, reading through RAM can be done. The block diagram and Verilog code of a RAM block is shown below.

 


Fig. 3: Single Port RAM

```
module ram(clk,addr,data_in,en,we,data_out);
input clk,en,we;
input[2:0] addr;
input[7:0] data_in;
output reg [7:0] data_out;
reg [7:0] mem [0:7];
initial begin data_out = 8'b00000000; end
always@(posedge clk)
if(en)begin
if(we)
mem[addr]=data_in;
else
data_out=mem[addr];
end
else
```

```
data_out = data_out;
```

```
endmodule
```

Dual port memory elements

The recent technology has developed dual port memories. Now it is possible to access the same address locations through two ports. Dual port memories have simplified many problems in designing digital systems. Both ROM and RAM can be of dual port. The block diagram of a true dual port RAM is shown below.

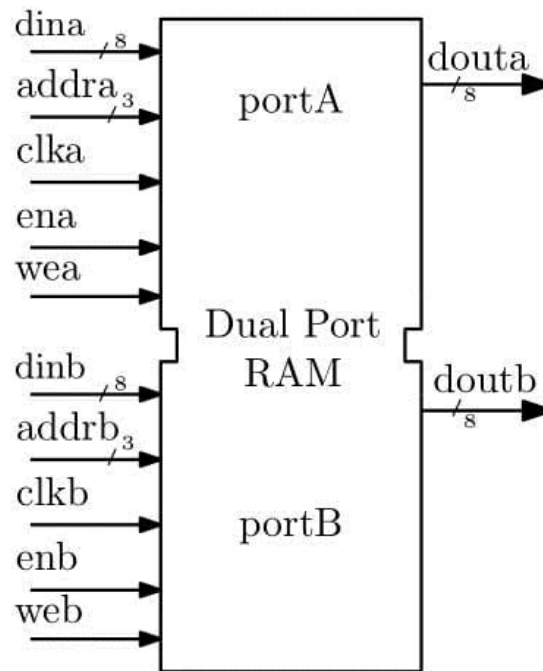


Fig. 4: Dual Port RAM

The dual port memories have separate control line for both the ports. The various modes of a typical true dual port RAM is shown below. In the mode 1, writing of data is possible through both the ports but not on the same location. In mode 3, data can be read through both the ports even from the same address location. In mode 2 and 3, one port is busy in writing while another port is reading data.

Table 1: Modes of Dual Port RAM

modes	ena	wea	enb	web	portA	portB
1	1	1	1	1	write	write
2	1	1	1	0	write	read
3	1	0	1	1	read	write
4	1	0	1	0	read	read

```
module dp_ram(clka,clkb,ada,adb,ina,inb,ena,enb,wea,web,outb,outb);

input clka,clkb,ena,wea,enb,web;

input[2:0] ada,adb;

input[7:0] ina,inb;

output reg [7:0] outa,outb;

reg [7:0] mem [0:7];

initial begin

outa = 8'b00000000;

outb = 8'b00000000;

end

always@(posedge clka)

if(ena)begin

if(wea)

mem[ada]=ina;

else

outa = mem[ada];

end

else

outa = outa;

always@(posedge clkb)

if(enb)begin

if(web)

mem[adb]=inb;

else

outb = mem[adb];

end

end
```

```
else
```

```
outb = outb;
```

```
endmodule
```

Similarly Dual Port ROM is also possible. The simple block diagram of a Dual Port ROM is

 


Fig. 5: Dual Port ROM

Realization of higher memory blocks

Higher capacity memory blocks can be realized using low capacity memory blocks by cascading. Realization of a 32×8 ROM using 8×8 memory blocks is shown below.

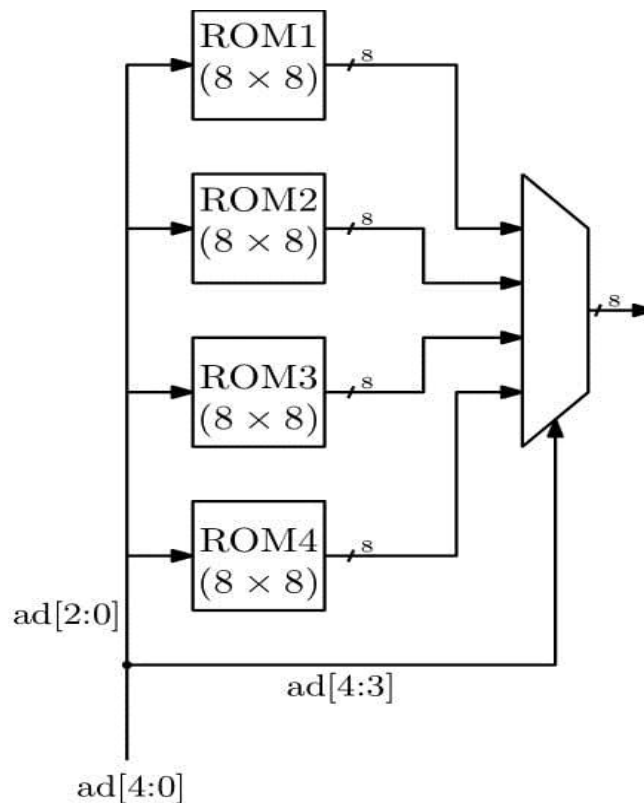


Fig. 6: Realization 32×8 ROM using 8×8 ROM (4 numbers)

Simple Dual Port RAM

A general question arises in mind that how the dual port RAMs are realized. A conceptual diagram of a simple Dual Port RAM having only 4-bit memory is shown below.

 


Fig. 7: Conceptual Diagram of a Simple Dual Port RAM

In a true Dual Port RAM writing can be done through both the ports. Also it has separate clock, en and we signals for separate port. In case of simple Dual Port RAM writing is done through port A and reading can be done through both the ports.

Note:

1. For storing constant data ROM should be used.
2. A dual port ROM is preferred over two single port ROMs.
3. Always use enable inputs to disable the memory blocks when not in use.

*More on memory blocks will be discussed in the post on FPGA implementation of digital systems.